

CPS213 – COMPUTER ORGANIZATION I

LAB #3

COMBINATIONAL CIRCUIT DESIGN

All students are required to answer the questions individually and hand in a paper copy of their written answers to TA during the first hour of the lab. Then continue with the simulation of the circuits and show the simulation results to TA.

Part A: A majority circuit is a combinational circuit whose output is equal to 1 if the input variables have more 1s than 0s. The output is 0 otherwise.

Design a 3-input majority circuit.

Simulate your design.

Part B: Design a logic circuit that provides the 2's complement of a 4-bit binary number. Simulate your design.

Part C: Design a 1-bit full adder using two 4-by-1 multiplexers. Simulate your design.